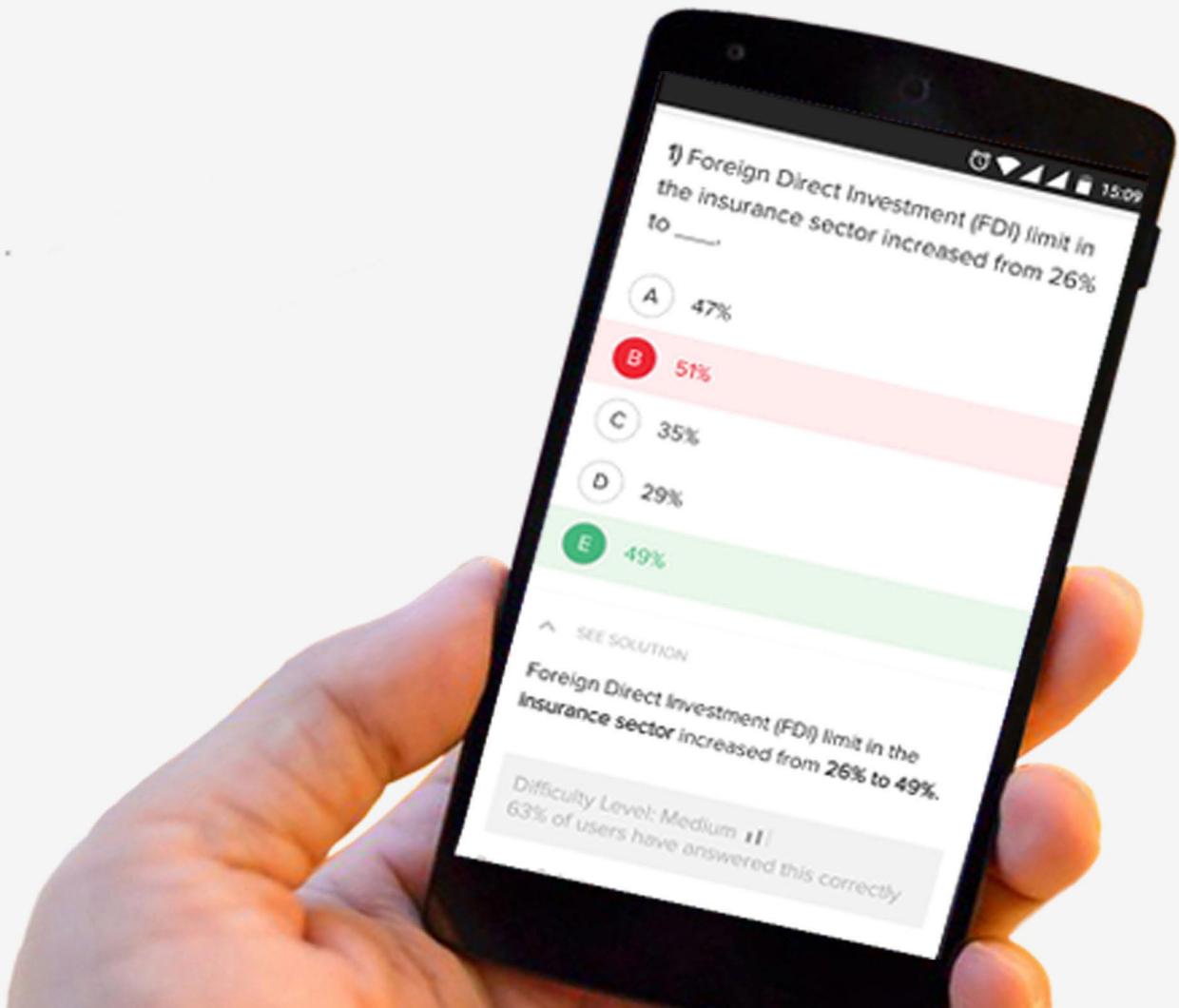




gradeup

# Formulas for Networks for GATE EC Exam



## Network Theory

**Current:** Electric current is the time rate of change of charge flow.


$$i = \frac{dq}{dt} \quad (\text{Ampere})$$

- Charge transferred between time  $t_0$  and  $t$


$$q = \int_{t_0}^t idt$$

**Sign Convention:** A negative current of  $-5\text{A}$  flowing in one direction is same as a current of  $+5\text{A}$  in opposite direction.

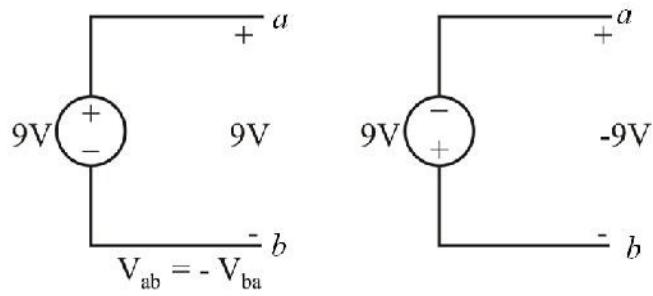**Voltage:** Voltage or potential difference is the energy required to move a unit charge through an element, measured in volts.



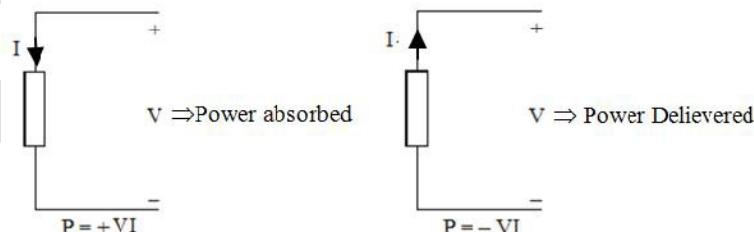**Power:** It is time rate of expending or absorbing energy.




- Law of conservation of energy must be obeyed in any electric circuit.
- Algebraic sum of power in a circuit, at any instant of time, must be zero.  
i.e.  $\sum P = 0$

### Circuit Elements:


**Passive element:** If it is not capable of delivering energy, then it is passive element. Example: Resistor, Inductor, and Capacitor

### Passive Elements

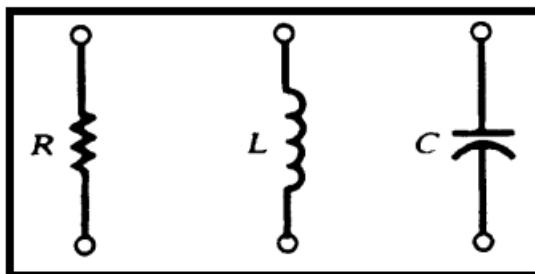

**Active element:** If an element is capable of delivering energy independently, then it is called active element. Example: Voltage source, and Current source.

### Active Elements

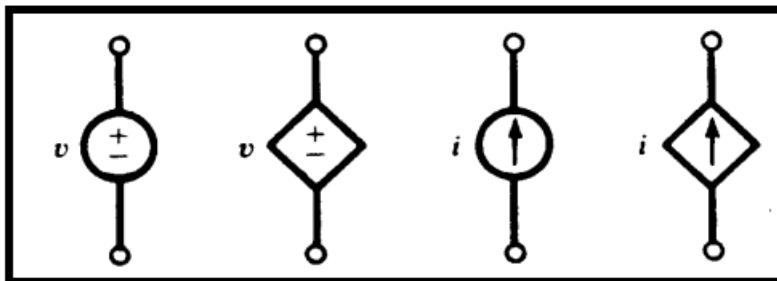

**Linear and Non linear elements:** If voltage and current across an element are related to each other through a constant coefficient then the element is called as linear element otherwise it is called as non-linear.

**Unidirectional and Bidirectional:** When elements characteristics are independent of direction of current then element is called bi-directional element otherwise it is called as unidirectional.

- R, L & C are bidirectional
- Diode is a unidirectional element.
- Voltage and current sources are also unidirectional elements.
- Every linear element should obey the bi-directional property but vice versa as is not necessary.

**Resistor:** Linear and bilateral (conduct from both direction)

- In time domain  $V(t) = I(t)R$
- In s domain:  $V(s) = RI(s)$

$$R = \frac{\rho l}{A} \text{ ohm}$$

- $l$  = length of conductor,  $\rho$  = resistivity,  $A$  = area of cross section

## Champion Study Plan - 2018

- Extension of wire to n times results in increase in resistance:

$$R' = n^2 R$$

- Compression of wire results in decrease in resistance:

$$R' = \frac{R}{n^2}$$

**Capacitor:** All capacitors are linear and bilateral, except electrolytic capacitor which is unilateral.

- Time Domain:

$$i(t) = \frac{C dv(t)}{dt} \quad v(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt$$

- In s-domain:

$$I(s) = sCV(s) \quad V(s) = \frac{1}{sC} I(s)$$

- Capacitor doesn't allow sudden change of voltage, until impulse of current is applied.
- It stores energy in the form of electric field and power dissipation in ideal capacitor is zero.

**Impedance:**

$$Z_c = -jX_c \Omega \quad \& \quad X_c = \frac{1}{\omega C}; \quad X_c \rightarrow \text{Capacitive reactance}; \quad \omega = 2\pi f$$

**Inductor:** Linear and bilinear element

**Time Domain:**  $v(t) = L \frac{di(t)}{dt} \quad i(t) = \frac{1}{L} \int_{-\infty}^t v(t) dt$

**Impedance**  $Z_L = jX_L \Omega \quad \& \quad X_L = \omega L \Omega$

**In s-domain**  $V(s) = sL I(s) \quad I(s) = \frac{1}{sL} V(s)$

- Inductor doesn't allow sudden change of current, until impulse of voltage is applied. It stores energy in the form of magnetic field.
- Power dissipation in ideal inductor is zero.

# Champion Study Plan - 2018

FORMULAS FOR THE BASIC CIRCUIT COMPONENTS					
CIRCUIT ELEMENT	IMPEDANCE		VOLT-AMP EQUATIONS		ENERGY (dissipated on R or stored in L, C)
	absolute value	complex form	instantaneous values	RMS values for sinusoidal signals	
RESISTANCE	R	R	v=i×R	Vrms=Irms×R	E=Irms <sup>2</sup> R×t
INDUCTANCE	2πfL	jωL	v=L×di/dt	Vrms=Irms×2πfL	E=Li <sup>2</sup> /2
CAPACITANCE	1/(2πfC)	1/jωC	i=C×dv/dt	Vrms=Irms/(2πfC)	E=Cv <sup>2</sup> /2







Notes:

R- resistance in ohms, L- inductance in henrys, C- capacitance in farads, f - frequency in hertz, t- time in seconds,  $\pi \approx 3.14159$ ;

$\omega = 2\pi f$  - angular frequency;



$j$  - imaginary unit ( $j^2 = -1$ )

Euler's formula:  $e^{j\omega t} = \cos \omega t + j \sin \omega t$

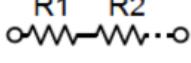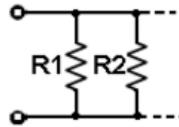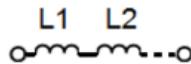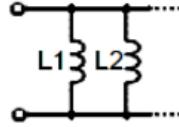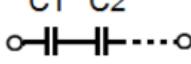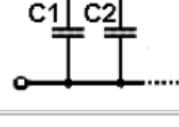EQUATIONS FOR SERIES AND PARALLEL CONNECTIONS					
CIRCUIT ELEMENT	SERIES CONNECTION			PARALLEL CONNECTION	
RESISTORS		Rseries =	$R_{series} = R_1 + R_2 + \dots$		$R_{parallel} = \frac{1}{(1/R_1 + 1/R_2 + \dots)}$
INDUCTORS		Lseries =	$L_{series} = L_1 + L_2 + \dots$		$L_{parallel} = \frac{1}{(1/L_1 + 1/L_2 + \dots)}$
CAPACITORS		Cseries =	$C_{series} = \frac{1}{(1/C_1 + 1/C_2 + \dots)}$		$C_{parallel} = C_1 + C_2 + \dots$

Rules of series	Rules of Parallel
$V_{eq} = v_1 + v_2 + v_3$ $R_{eq} = R_1 + R_2 + R_3$ $C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$	$i_{eq} = i_1 + i_2 + i_3$ $R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$ $C_{eq} = C_1 + C_2 + C_3$


## Champion Study Plan - 2018

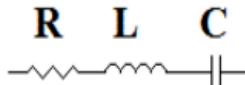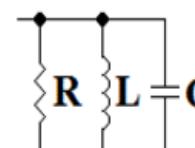CALCULATIONS OF EQUIVALENT RLC IMPEDANCES		
CIRCUIT CONNECTION	COMPLEX FORM	ABSOLUTE VALUE
<b>Series</b> 	$Z = R + j\omega L + 1/j\omega C$	$Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$
<b>Parallel</b> 	$Z = \frac{1}{(1/R + 1/j\omega L + j\omega C)}$	$Z = \frac{1}{\sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2}}$
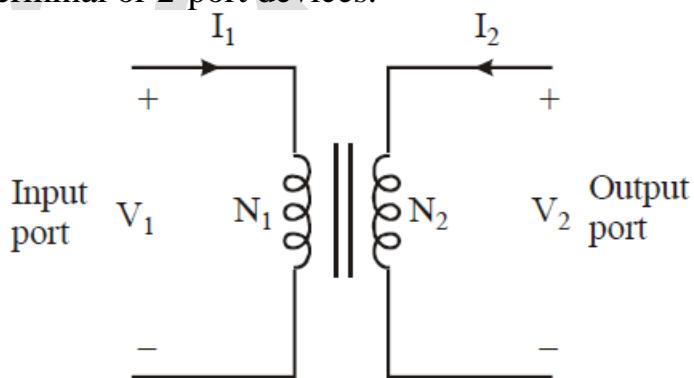
### Mesh Analysis:

- Path - A set of element that may be traversed in order, without passing thru the same node twice
- Loop - a closed path
- Mesh - A loop that does not contain any other loop within it
- Planar Circuit - A circuit that may be drawn on a plane surface in such a way that there are no branch crossovers
- Non-Planar Circuit - A circuit that is not planar, i.e, some branch(es) pass over some other branch(es) (Can not use Mesh Analysis)

**Transformer:** 4 terminal or 2-port devices.



- $N_1 > N_2$  : Step down transformer

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$


- $N_2 > N_1$  : Step up transformer

$$\frac{I_1}{I_2} = \frac{N_2}{N_1}$$

Where  $\frac{N_1}{N_2} = K \rightarrow \text{Turns ratio.}$

- Transformer doesn't work as amplifier because current decreases in same amount power remain constant.


### **Gyrator:**

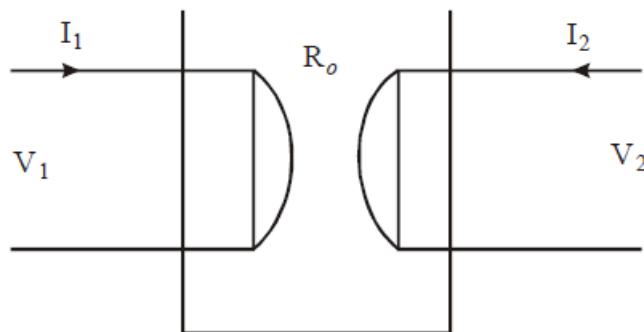

- $R_0$  = Coefficient of Gyrator
- $V_1 = R_0 I_2$
- $V_2 = -R_0 I_1$
- If load is capacitive then input impedance will be inductive and vice versa.
- If load is inductive then input impedance will be capacitive.
- It is used for simulation of equivalent value of inductance.
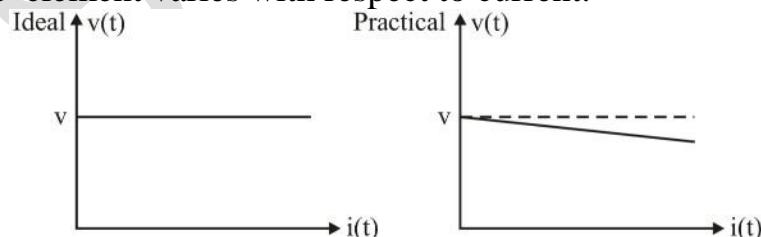
### **Voltage Source:**


- In practical voltage source, there is small internal resistance, so voltage across the element varies with respect to current.



- Ideal voltmeter,  $R_v$  is infinite (Internal resistance)
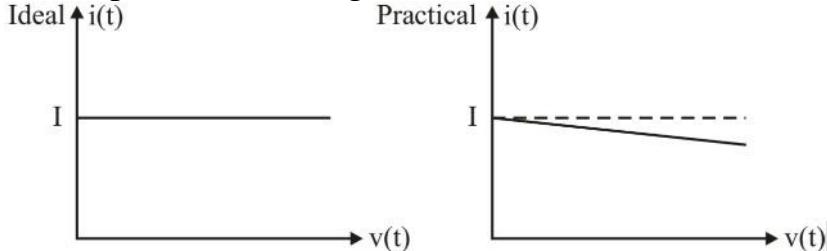
## Current Source:

- In practical current source, there is small internal resistance, so current varies with respect to the voltage across element



- Ideal Ammeter,  $R_a$  is 0 (Internal resistance)
- Internal resistance of voltage source is in series with the source.
- Internal resistance of ideal voltage source is zero.
- Internal resistance of current source is in parallel with the source.
- Internal resistance of ideal current source is infinite.

**Independent Source:** Voltage or current source whose values doesn't depend on any other parameters.

- Example: Generator

**Dependent Source:** Voltage or current source whose values depend upon other parameters like current, voltage.

**Lumped Network:** A network in which all network elements are physically separable is known as lumped network.

**Distributed network:** A network in which the circuit elements like resistance, inductance etc, are not physically separate for analysis purpose, is called distributed network. Example: Transmission line.

**Thevenin's Theorem:** Any linear network can be replaced by an independent voltage sources in series with an impedance such that the current voltage relation at the terminals is unchanged.

**Norton's Theorem:** Identical to thevenin's statement except that the equivalent circuit is an independent current source in parallel with an impedance. ( $Z_S = R_{Th}$ )

### Average Power

$$P_{Avg} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} \cos(\theta)$$

or  $= V_{rms} I_{rms} \cos(\theta)$

### Power Factor

$$PF = \cos(\theta)$$

$$\theta = \theta_V - \theta_i$$

### Reactive power

$$Q = V_{rms} I_{rms} \sin(\theta)$$

Measured *VARs*

Volt Amperes Reactive

$$P^2 + Q^2 = (V_{rms} I_{rms})^2$$

### Apparent Power (S)

$$S = V_{rms} I_{rms} = Va$$

$$S = P + j\bar{Q}$$

$$S = I^2 Z$$


### Maxpower Transfer

$$Z_L = R_L + jX_L$$

$$= R_{Th} - jX_{Th} = Z_{Th}$$

### True Power

$$P = I^2 R$$

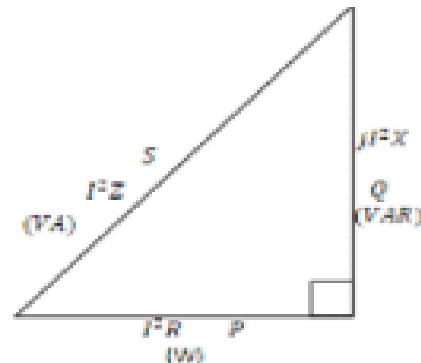

### Root Mean Square

Average of a signal that is symmetric about the horizontal Axis

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$




$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$V_{eff} = V_{rms}$$

$$I_{eff} = I_{rms}$$

## Champion Study Plan - 2018

---

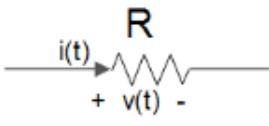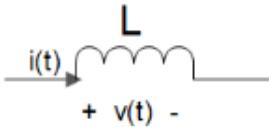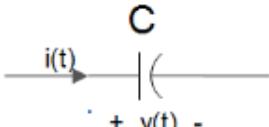Time Domain	Frequency domain
 $R$	$v = Ri$ $V = RI$
 $L$	$v = L \frac{di}{dt}$ $V = j\omega LI$
 $C$	$v = \frac{1}{C} \int i dt$ $V = \frac{1}{j\omega C} I$

grade



## Banking, SSC, GATE, JEE, NEET & other Online Mock Test Series

- Based on Latest Exam Pattern
- Available in Hindi & English
- Get all India rank & result analysis
- Detailed Solutions
- Can be taken on web & mobile

